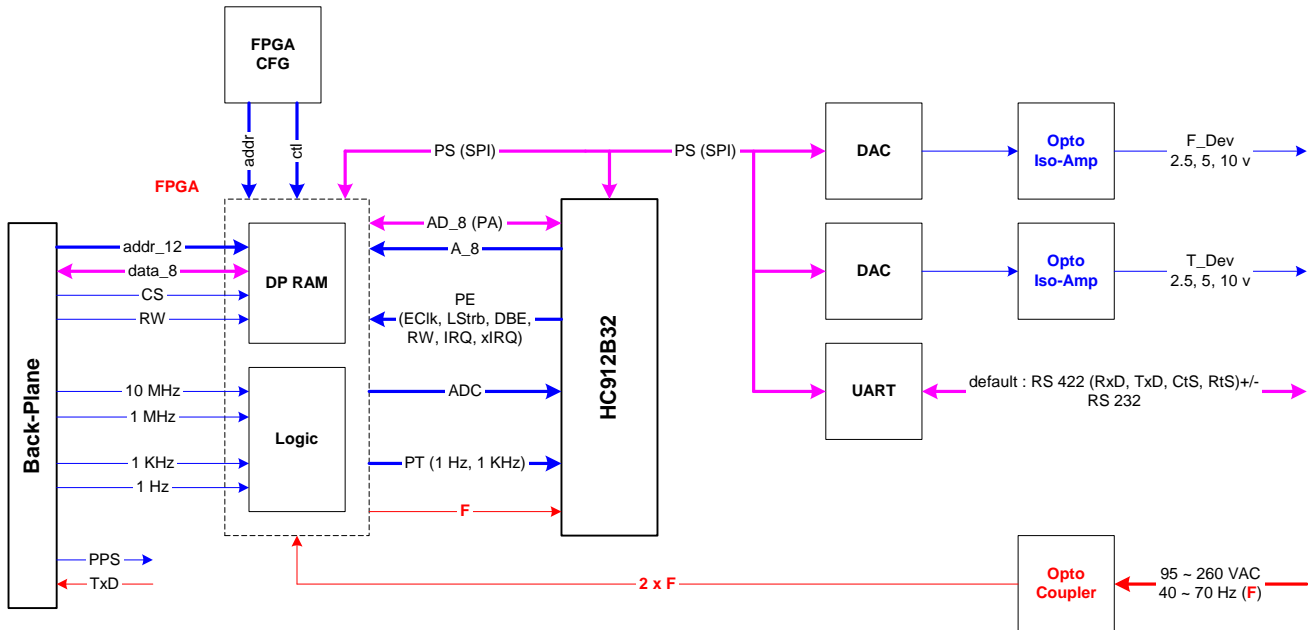


Notes on Design of Frequency and Time Deviation Monitor


©Duy-Ky Nguyen

15 May 2003


1.1.1. Block Diagram



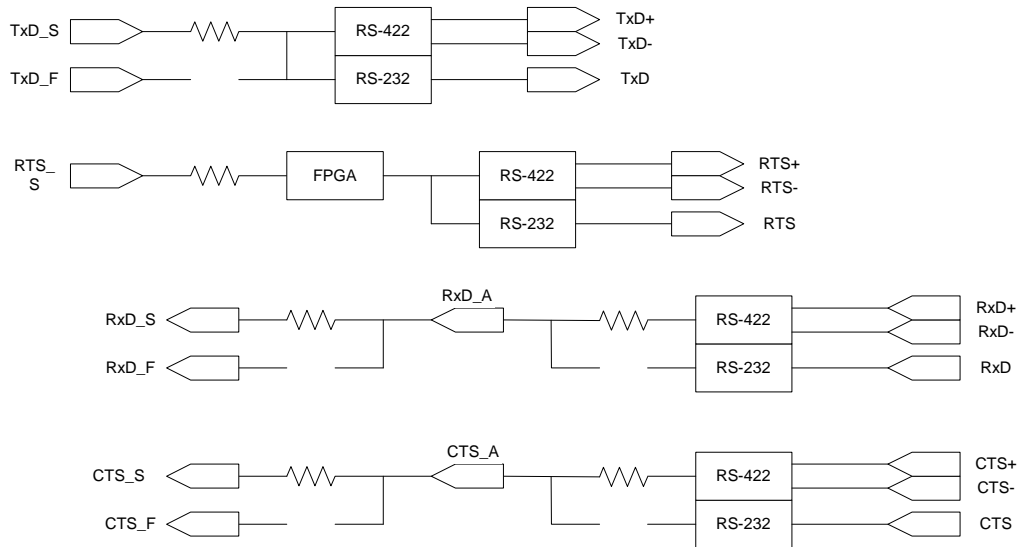
- 1) Parallel CFG FPGA
 - Mode M[2:0] = 3'b110
 - CLLK : 16 MHz
 - CDAT : separate 8-bit data
 - CS = WS = 0
 - PRG, INIT (Reset), DONE
 - TDI_F (c); TD_F (TDO.c – TDI.f), TDO_F (f)
- 2) HC912B32 includes (i) 32 KB Flash for code, (ii) 728 B EEPROM for constant (baud, 50/60 Hz, ...)
 - There are no PU/PD resistors for unused IO pins. They are input after reset. SW is expected to set them output for noise immunity.
- 3) SW selects either SPI or multiplexed AD to access DPRAM in FPGA.
- 4) Unused pins of HC12 (PDLC) and FPGA are connected to header in case of connection using ribbon cable for testing purpose;
- 5) Serial Comm has HW hand-shake CTS RTS (default with MAX3100)
- 6) There are 3 ranges for T/F deviation outputs: 2.5, 5 and 10 v selectable using jumper.




2. Power-Line Monitor

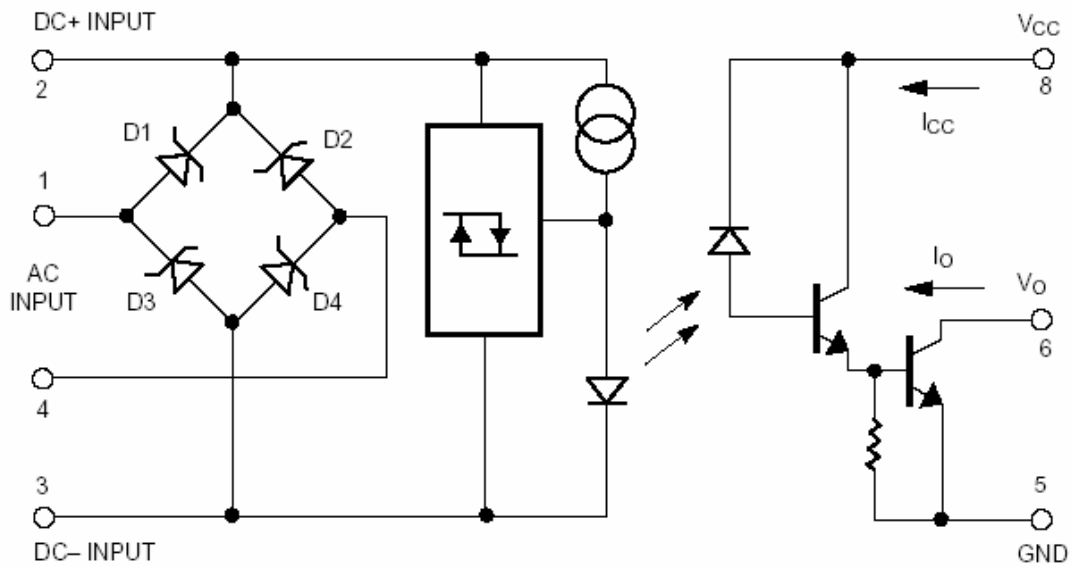

 Block Diagram of the **HCPL-3700 (Agilent Tech)**



 Interfacing an AC Voltage to an MPU using the HCPL-3700., $V = 115 \text{ VAC}$, $P_R = 116 \text{ mW}$ (2.5 mA)



Output Waveforms of the HCPL-3700 Design in Figure 7 with no Filtering Applied, $V_{CC} = 2 \sim 18\text{ V}$

Design

Input 110 ~ 240 VAC, so the mode of Input Clamp Voltage is chosen with pins 2 & 3 open. Therefore we have following typical params

$$V_{IHC2} = |V_1 - V_4| = 6.7\text{ V}$$

$$|I_{IN}| = 10\text{ mA}$$

$$V_{peak} = 240 * 1.414 = 339.4\text{ V}$$


So

$$R_X = (V_{peak} - V_{IHC2}) / |I_{IN}| = 33.27\text{ KOhm}$$

3. Opto-Coupler

3.1. AC Interface

Using HCPL-3700 from Agilent Technology.

 

For the mode of Input Clamp Voltage, we have

$$V_{IHC2} = 6.7\text{ v}$$

$$|I_{in}| = 10\text{ mA}$$

we have

$$V_r = V_{pk} - V_{IHC2} = 240 * 1.414 - 6.7 = 332.7\text{ v}$$

So

$$R_x = V_r / |I_{in}| = 332.7 / 10 = 33.3\text{ K}$$

$$R_{x/2} = 16.7\text{ K}$$

Use $R_{x/2} = 18.7\text{ K}$, 1%, so

$$P_{x/2} = (V_r/2)^2 / R_{x/2} = 1.5\text{ w}$$

Choose


$$R_{x/2} = 18.7\text{ K}, 1\%, 1.5\text{ w}$$

Question:

Div2 is a flip-flop to divide 120 Hz for 60 Hz
 RL is not required ???

3.2. Isolation Amplifier

Using HCNR-0201 from Agilent Technology.

 

Data sheet gives $I_F = 1 \sim 20$ mA, choose $I_F = 2$ mA, we have

$$R_3 = (V_{CC} - V_F) / I_F = 5 / 2 = 2.5 \text{ K}$$

Data sheet gives

$$I_{PD1} = K_1 * I_F = 0.5 * 2 = 1 \text{ mA}$$

so

$$R_1 = V_{IN} / I_{PD1} = 5 / 1 = 5 \text{ K}$$

as V_{IN} is an analog signal out of a 5-v DAC (Digital Analog Converter)

Data sheet gives

$$I_{PD2} = K_3 * I_{PD1} = 1 * 1 = 1 \text{ mA}$$


so

$$R_2 = V_{CC} / I_{PD2} = 5 / 1 = 5 \text{ K}$$

C_1 is for $C_1 R_1$ to meet F_{max}

C_2 is for $C_2 R_2$ to meet F_{max}

4. Op-Amp

 

Ideal Op-Amp has the following characteristics

$$V_- = V_+ \tag{1}$$

and

$$I_+ = I_- = 0 \tag{2}$$

Eqs (1) & (2) give

$$\frac{G_1 V_1 + G_3 V_0}{G_1 + G_3} = \frac{G_2 V_2}{G_2 + G_4} \Rightarrow \frac{G_3 V_0}{G_1 + G_3} = \left(\frac{G_2 V_2}{G_2 + G_4} - \frac{G_1 V_1}{G_1 + G_3} \right) \Rightarrow \frac{V_0}{1 + G_1 / G_3} = \left(\frac{V_2}{1 + G_4 / G_2} - \frac{V_1}{1 + G_3 / G_1} \right)$$

or

$$V_0 = \left(1 + G_1/G_3\right) \left(\frac{V_2}{1 + G_4/G_2} - \frac{V_1}{1 + G_3/G_1} \right) = \left(1 + R_3/R_1\right) \left(\frac{V_2}{1 + R_2/R_4} - \frac{V_1}{1 + R_1/R_3} \right)$$

or

$$V_0 = -\frac{R_3}{R_1} V_1 + \left(1 + \frac{R_3}{R_1}\right) \left(\frac{R_4}{R_2 + R_4} \right) V_2 \tag{3}$$

We want $V_0 = -10 \sim +10$ v, so we want $0 \sim -20$ v for 1st term, and $+10$ v for 2nd. Therefore, for $V_1 = 0 \sim 2.5$ v we have

$$\frac{R_3}{R_1} = 8$$


thus, for $V_2 = 2.5$ v, we have

$$(1 + 8) \frac{R_4}{R_2 + R_4} 2.5 = 10 \Rightarrow \frac{R_2}{R_4} = \frac{9 * 2.5}{10} - 1 = 1.25 = \frac{5}{4}$$


Note that these equations cannot be solved for non-inverting mode $0 \sim +20$ v.


5. SPI interface between HC12 and FPGA

5.1. Requirements

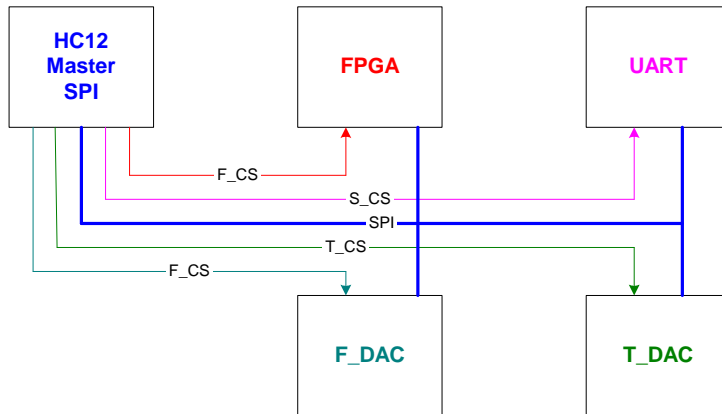


 HC12 has master SPI interface with FPGA, DAC and UART. HC12 has 4 selectable SPI modes, but DAC and UART has only one that is CPOL=0, CPHA=0 in HC12. So FPGA will be implemented the same.



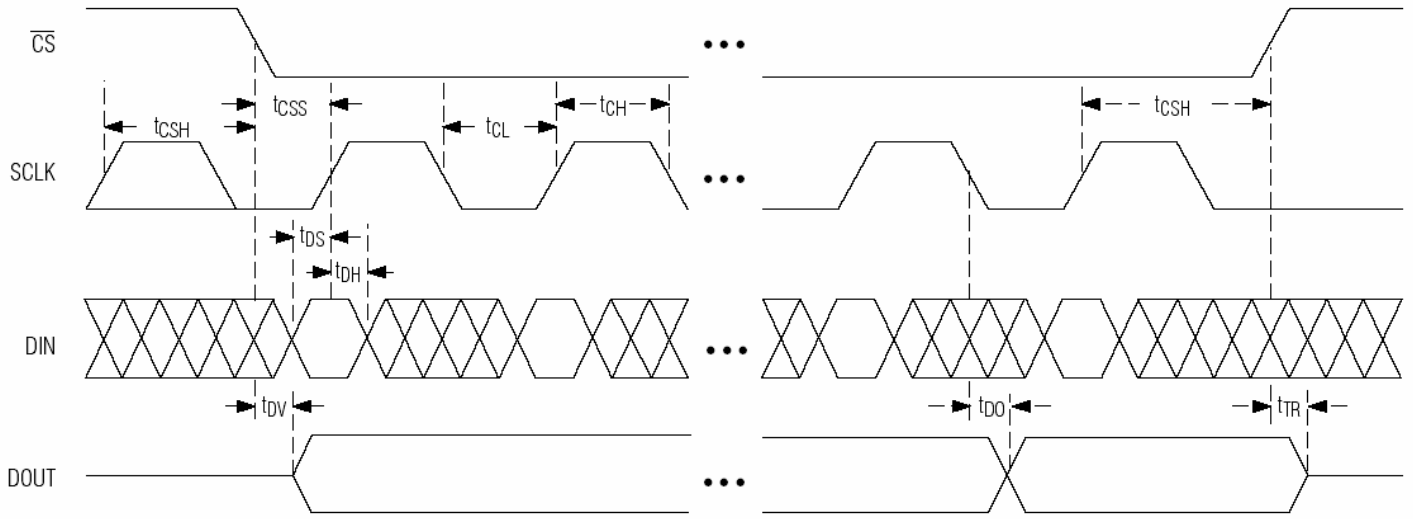


SPI of UART MAX-3100

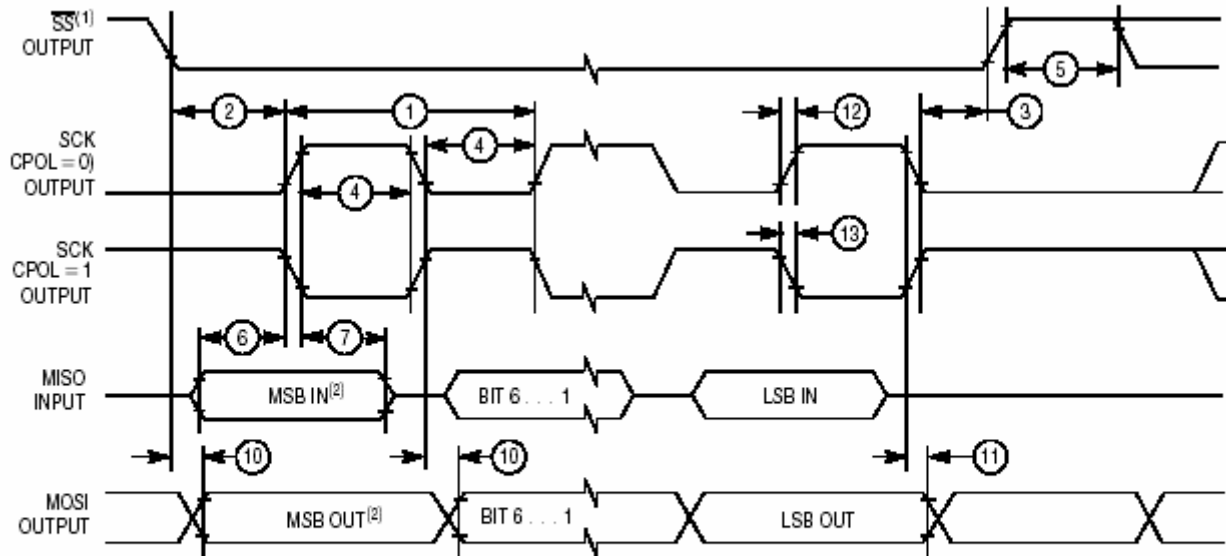

Notes:

1. SS output mode (DDS7 = 1, SSOE = 1).
2. LSBF = 0. For LSBF = 1, bit order is LSB, bit 1, ..., bit 6, MSB.

A) SPI Master Timing (CPHA = 0)

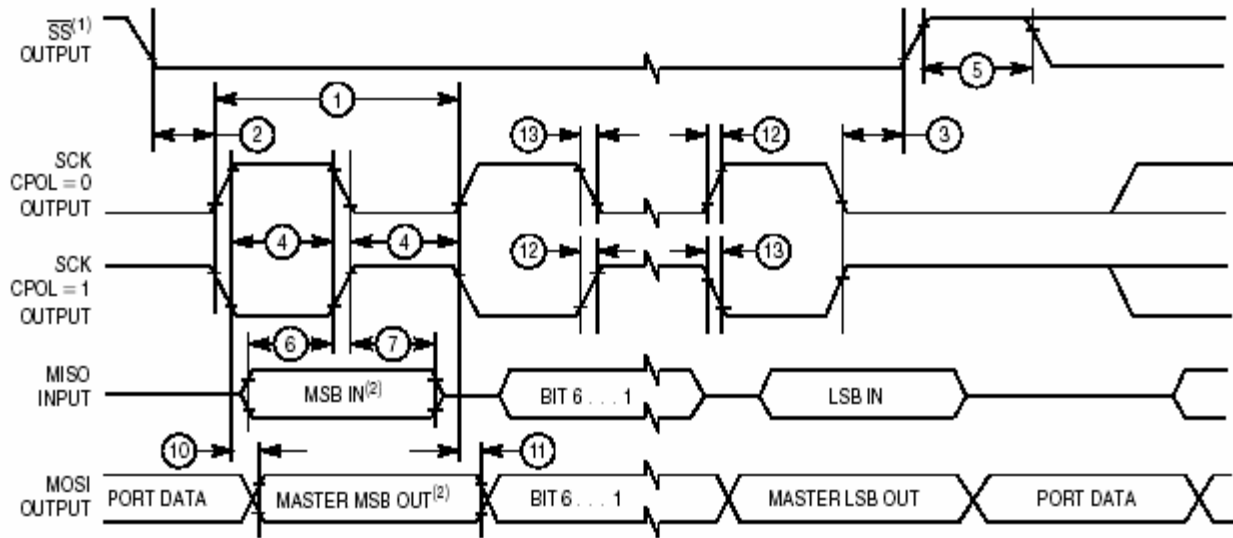


Notes:

1. \overline{SS} output mode (DDS7 = 1, SSOE = 1).
2. LSBF = 0. For LSBF = 1, bit order is LSB, bit 1, ..., bit 6, MSB.



B) SPI Master Timing (CPHA = 1)



Num	Function(1)	Symbol	Min	Max	Unit
	Operating frequency	fOP	DC	1/2	E-clock frequency
1	SCK period	tSCK	2	256	tcyc
2	Enable lead time	tLead	1/2	—	tsck
3	Enable lag time	tLAG	1/2	—	tsck
4	Clock (SCK) high or low time	tWSCK	tcyc 30	128 tcyc	ns
5	Sequential transfer delay	tTD	1/2	—	tsck
6	Data setup time (inputs)	tSU	30	—	ns
7	Data hold time (inputs)	tHI	0	—	ns
8	Slave access time	tA	—	1	tcyc
9	Slave MISO disable time	tDIS	—	1	tcyc
10	Data valid (after SCK edge)	tV	—	50	ns
11	Data hold time (outputs)	tHO	0	—	ns
12	Rise Time				
	Input	tRI	—	tcyc 30	ns
	Output	tRO	—	30	ns
13	Fall Time				
	Input	tFI	—	tcyc 30	ns
	Output	tFO	—	30	ns


Below is expected SPI signals

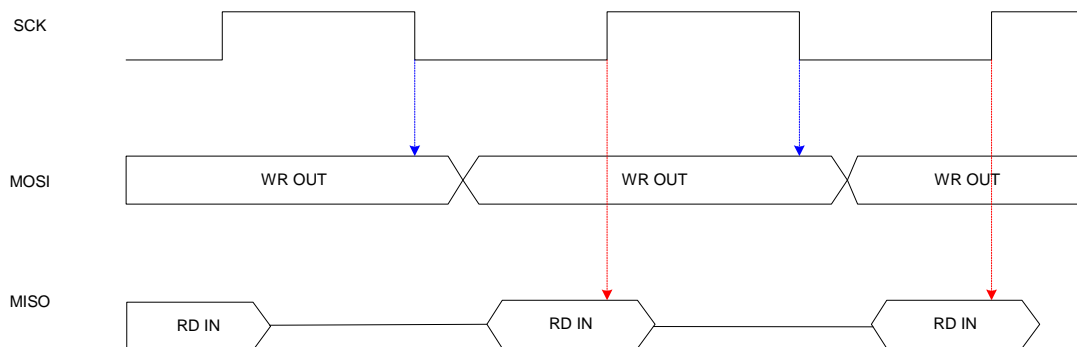

5.2. Implementation

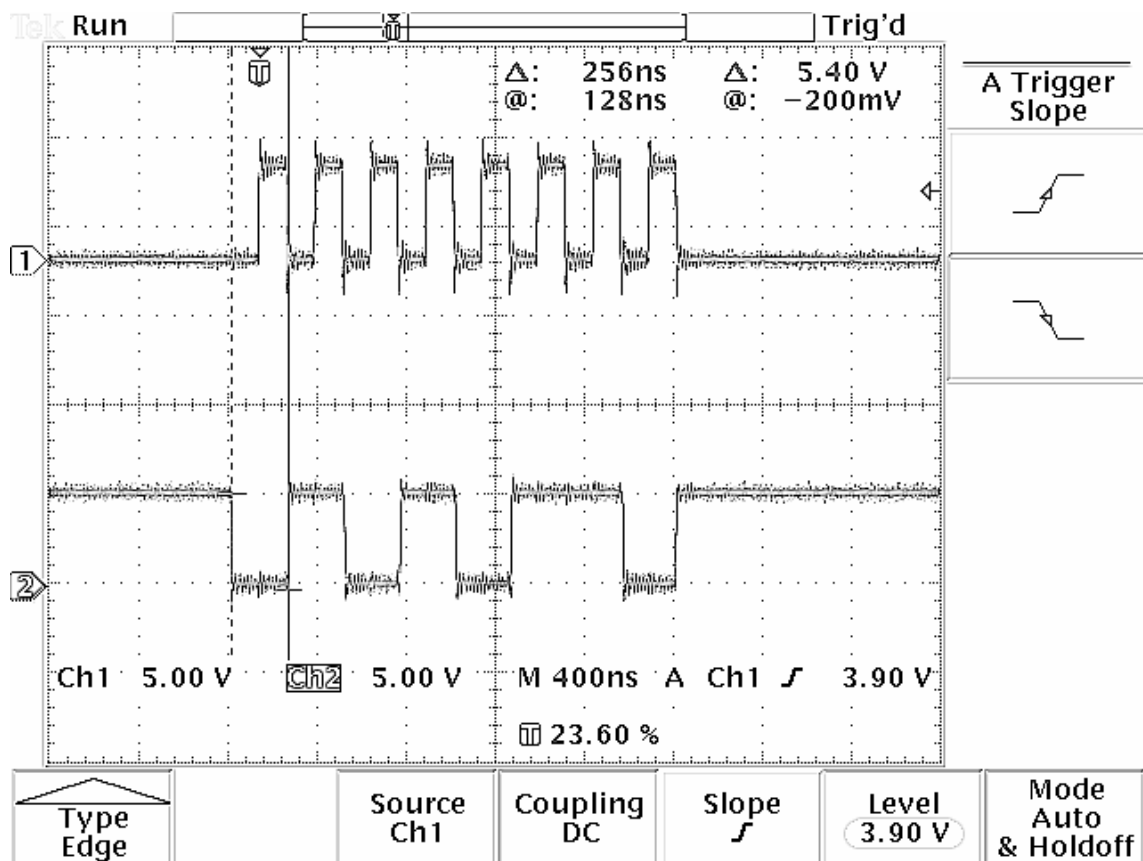 

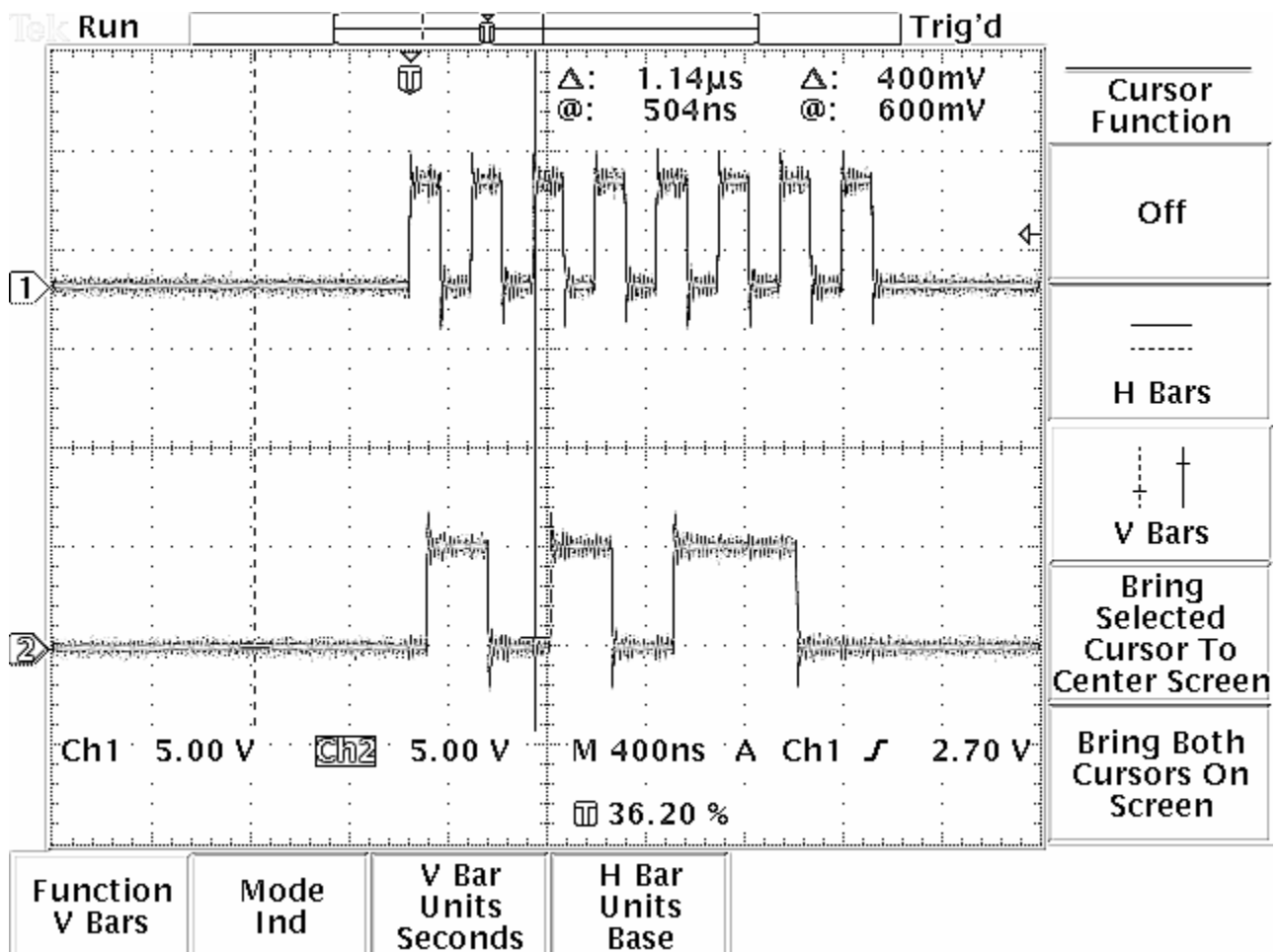 

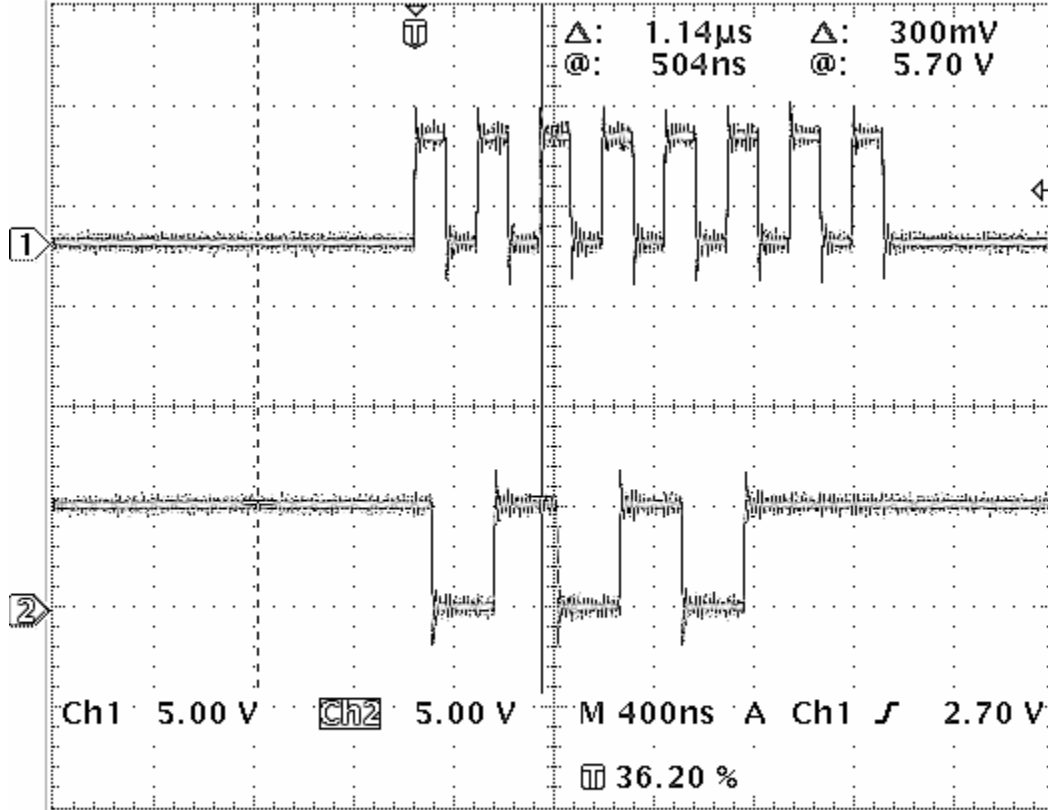

- Cursor Function**
- Off
 - H Bars
 - V Bars
 - Bring Selected Cursor To Center Screen
 - Bring Both Cursors On Screen

Function V Bars	Mode Ind	V Bar Units Seconds	H Bar Units Base
--------------------	-------------	---------------------------	------------------------

